



Srishyla Educational Trust (R)

GM INSTITUTE OF TECHNOLOGY

Approved by AICTE | Affiliated to V.T.U.Belgaum | Recognized by Govt. of Karnataka



Member of
NASSCOM

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Subject: Introduction to Electronics Engineering

Sem: I 'B'

Assignment Questions-2 (Module 2 -Part A)

1. Explain the pin configuration of an OPAMP. Mention the OPAMP ideal characteristics.
2. Explain the OPAMP parameters
3. Draw neat circuit diagram, input output waveforms and output voltage expressions of the following OPAMPs i) inverting amplifier, ii) non-inverting amplifier, iii) differentiator iv) integrator and v) summing amplifier.
4. Explain the following with a neat diagram
a) comparator (b) a differentiator (c) an integrator (d) Inverting Amplifier e) Voltage follower